

Computer Architecture

Digital Circuits

<http://d3s.mff.cuni.cz/teaching/nswi143>



Lubomír Bulej

bulej@d3s.mff.cuni.cz

CHARLES UNIVERSITY IN PRAGUE

faculty of mathematics and physics

Digital computer

- **Two voltage levels of interest**
 - **High level**
 - Logical one (signal *high/true/asserted*)
 - **Low level**
 - Logical zero (signal *low/false/deasserted*)
 - Logical values are complementary and inverse of each other
 - Unlike the voltage levels representing logical ones and zeros



Logic blocks



- **Combinational**

- No memory → no internal state
- Output depends only on current input
- Represents logical functions

- **Sequential**

- Has memory → has internal state
- Output depends on input and internal state
- Captures sequence of steps



Logic functions and truth tables

- **Logic function (also Boolean function)**
 - Output value is a function of input values
 - $f: \mathbf{B}^k \rightarrow \mathbf{B}$, where $\mathbf{B} = \{0, 1\}$ and $k \in \mathbf{N}$ is arity
 - Truth table
 - Function defined by enumerating the output for each combination of inputs (a table 2^k rows for k inputs)

Inputs		Output
a	b	$f(a, b)$
0	0	0
0	1	1
1	0	1
1	1	1



Boolean algebra

- **Logic functions expressed as equations**
 - Variables hold values from $\mathbf{B} = \{0, 1\}$
 - Basic operators – primitive logic functions
 - **Logical inversion (NOT):** $\bar{x}$, $\neg x$, $!x$
 - **Logical product, conjunction (AND):** $x \cdot y$, $x \wedge y$, $x \&\& y$
 - **Logical sum, disjunction (OR):** $x + y$, $x \vee y$, $x || y$
 - Additional operators (16 for 2 variables)
 - NAND, NOR, XOR etc.



Logic operators

Inputs		Basic operators			Universal operators	
a	b	NOT a	a AND b	a OR b	a NAND b	a NOR b
		$\neg$	$\wedge$	$\vee$	$\uparrow$	$\downarrow$
0	0	1	0	0	1	1
0	1	1	0	1	1	0
1	0	0	0	1	1	0
1	1	0	1	1	0	0

Inputs		Other operators						
a	b	a XOR b	a XNOR b					
		$\oplus$	$\leftrightarrow$	$\rightarrow$	$\leftarrow$	$\dots$	$\perp$	$\top$
0	0	0	1	1	1	$\dots$	0	1
0	1	1	0	1	0	$\dots$	0	1
1	0	1	0	0	1	$\dots$	0	1
1	1	0	1	1	1	$\dots$	0	1



Boolean algebra laws

- **Idempotency:** $a + a = a, a \cdot a = a$
- **Computativity:** $a + b = b + a, a \cdot b = b \cdot a$
- **Associativity:** $a + (b + c) = (a + b) + c, a \cdot (b \cdot c) = (a \cdot b) \cdot c$
- **Absorption:** $a \cdot (a + b) = a, a + (a \cdot b) = a$
- **Distributivity:** $a \cdot (b + c) = (a \cdot b) + (a \cdot c), a + (b \cdot c) = (a + b) \cdot (a + c)$
- **Neutrality of 0 and 1:** $a + 0 = a, a \cdot 1 = a$
- **Aggressivity of 0 and 1:** $a + 1 = 1, a \cdot 0 = 0$
- **Complementarity:** $a + \neg a = 1, a \cdot \neg a = 0$
- **Absorption of negation:** $a \cdot (\neg a + b) = a \cdot b, a + (\neg a \cdot b) = a + b$
- **De Morgan's laws:** $\neg(a + b) = \neg a \cdot \neg b, \neg(a \cdot b) = \neg a + \neg b$
- **Double negation:** $\neg(\neg a) = a$



Intermezzo: CPU logical operations (1)

- Logic functions extended to operate on (finite) sequences of bits
 - Word = finite sequence of bits
 - Word length = number of bits in the sequence
 - Output of a logic operation a is function of input values
 - $f: (\mathbf{B}^n)^k \rightarrow \mathbf{B}^n$, where $\mathbf{B} = \{0, 1\}$, $k \in \mathbf{N}$ is arity and $n \in \mathbf{N}$ is word length



Intermezzo: CPU logical operations (2)

- **(Bitwise) logical product/sum/inversion**
 - Operators $\&$, $|$, $\sim$ etc. in C-like languages
 - Primitive logic function applied to individual bits of the input words, result stored to individual bits of the output word
 - Allow isolating (AND), zeroing (AND, NOR), setting (OR), inverting (XOR) selected bits, or inverting all bits (NOT), of the input word






Intermezzo: CPU logical operations (3)

- **Logical shifts (left and right)**
 - Operators `<<` and `>>` in C-like languages
 - Shifts bits in a words i positions to the left or right
 - “Vacated” bits are replaced with 0
 - For binary natural numbers
 - Shift by i bits to the left $\rightarrow$ multiplying by 2^i
 - Shift by i bits to the right $\rightarrow$ dividing by 2^i



Logic gates (1)

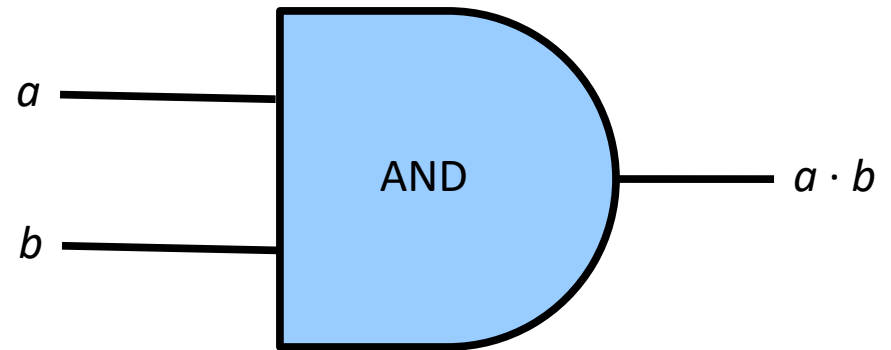 
 
- **Physical implementation basic logic functions**
 - Basic gates: NOT, OR, AND



Logic gates (2)

- **Physical implementation of logic operators**

  - Inverting gates: NAND, NOR
- Less common gates: XOR



Combinational logic circuits

- **Implementation of more complex logic functions**
 - Combines multiple logic operators
 - Logic signals correspond to variables
 - Logic gates correspond to primitive operators
 - Most commonly NAND or NOR gates
 - Sufficient for expressing any logic function
- **Logic block**
 - Abstracts away from internal structure of a circuit
 - Provides functional building blocks



Logic blocks: binary (half) adder

- **Adds two 1-bit numbers**

- The simplest case

- **Input:**


- operand a
- operand b

- **Output:**

- sum s
- carry c

- **Function:**

 
- $s = a \cdot \neg b + \neg a \cdot b = a \text{ XOR } b$
- $c = a \cdot b = a \text{ AND } b$



Inputs		Outputs	
a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0




Logic blocks: binary (half) adder (2)

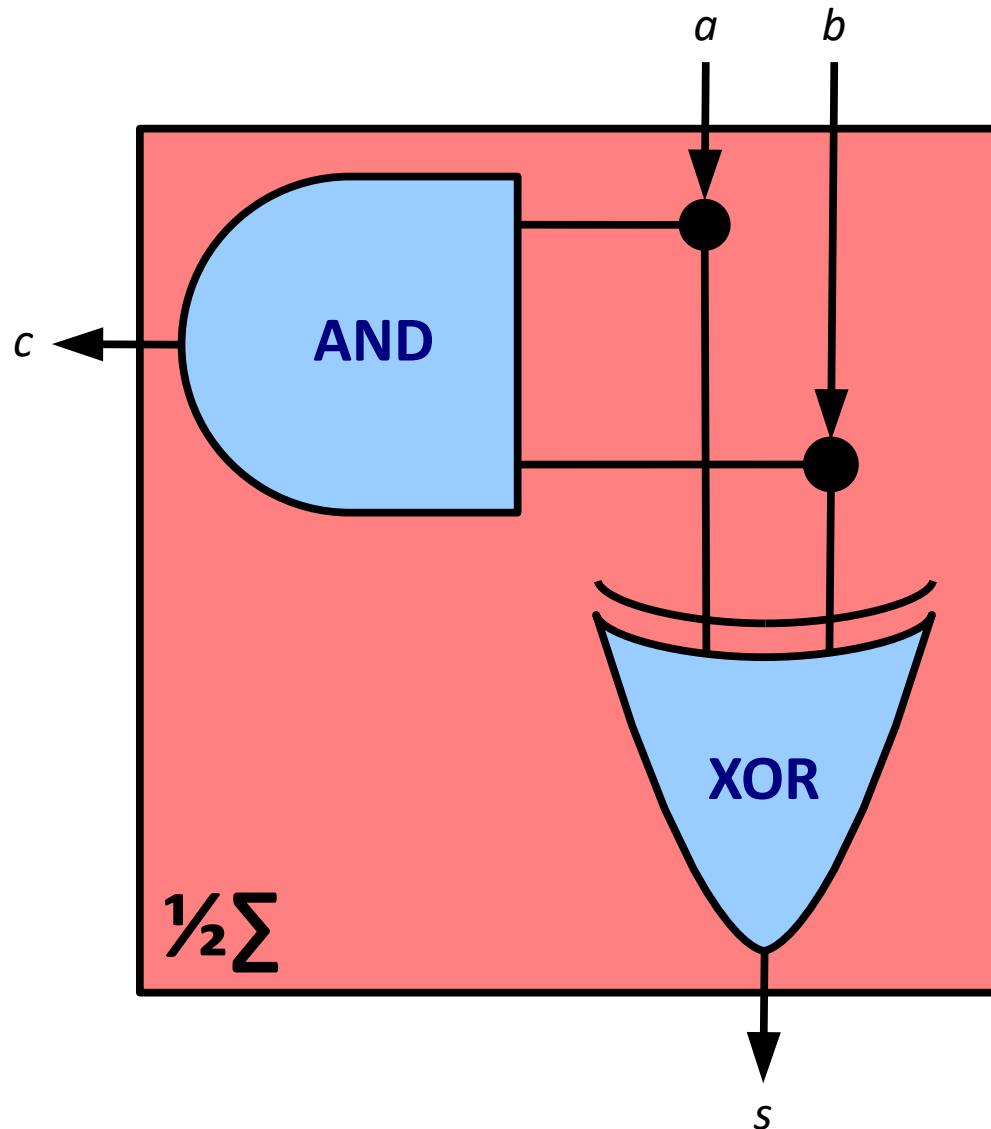

Logic blocks: binary adder (3)

- Adding n -bit numbers

 - Merge n $\frac{1}{2}$ -adders for individual bits?



- $\frac{1}{2}$ -adder cannot propagate carry from previous additions (not enough inputs)



Logic blocks: binary adder (4)

- **Full adder**


- Adds two 1-bit numbers taking into account carry from previous addition

- **Input:**

- operand a
- operand b
- carry c_0

- **Output:**

- sum s
- carry c

 

Logic blocks: binary adder (5)

● Full adder

- Adds two 1-bit numbers taking into account carry from previous addition
- **Inputs:** operand ***a***, operand ***b***, carry ***c*₀**

- **Outputs:** sum ***s***, carry ***c***

- $s = \neg c_0 \cdot (a \cdot \neg b + \neg a \cdot b) + c_0 \cdot (a \cdot b + \neg a \cdot \neg b)$

$$s = \dots$$

$$s = c_0 \text{ XOR } (a \text{ XOR } b)$$


- $c = a \cdot b + c_0 \cdot (a \cdot \neg b + \neg a \cdot b)$

$$c = (a \text{ AND } b) \text{ OR } (c_0 \text{ AND } (a \text{ XOR } b))$$

c_0	a	b	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



Logic blocks: binary adder (6)

 


Logic blocks: binary adder (7)




Abstraction:


$$a + b + c_0 = (a + b) + c_0$$

 

Logic blocks: binary adder (8)

 

Function block:

 


Logic block for subtraction

- **Taking advantage of 2's complement**
 - Basic building block: adder
 - Use XOR gate as a controlled inverter
 - **Example:** 2-bit ALU supporting addition and subtraction
 - **Data input:** operand bits a_1a_0 , operand bits b_1b_0
 - **Control input:** signal **SUB** to determine operation
 - $SUB = 0 \rightarrow$ addition
 - $SUB = 1 \rightarrow$ subtraction
 - **Output:** sum/difference bits s_1s_0 , carry c




2-bit ALU for adding/subtracting

 $SUB = 1$ inverts bits of the second operand and adds 1 (negates number)




Sequential logic

 - **Combinational logic + memory elements**
 - Memory elements keep internal state
 - Inputs and the contents of memory (internal state) determines outputs and next internal state
 - Synchronous vs. asynchronous sequential circuits
 - Determines how and when state changes
 - Need to ensure stable inputs (inputs don't change)




Synchronous sequential circuits

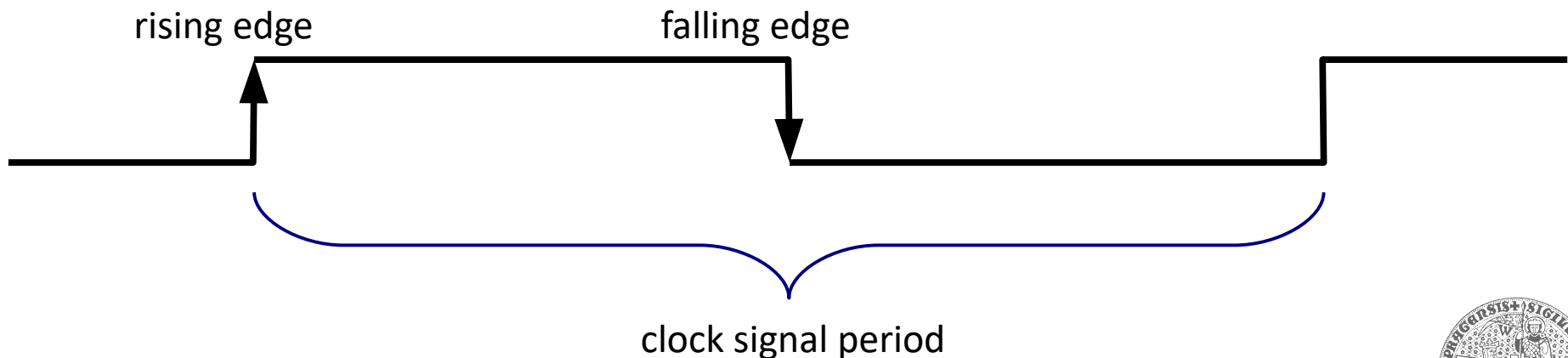- **Clock signal to synchronize state changes**
 - Change state during one clock cycle
 - Inputs of combinational logic does not change while it is being read
 - Writing of values from outputs to memory elements happens with rising/falling edge of the clock signal




Memory elements

 - **Pair of inverters with feedback**
 - Asynchronous circuit with two stable states
 - Allows “storing” 1 bit of information
 - We just need to be able to control the state...
 - We need a gate that can pass signal unchanged, but allows forcing a value if needed
 - Basic building block for memory elements




Set-Reset (R-S) latch, NOR-based

 

Vstupy		Výstupy	
r	s	q_n	$\bar{q}_n$
0	0	q_{n-1}	$\neg q_{n-1}$
0	1	1	0
1	0	0	1
1	1	?	?



Set-Reset (R-S) latch, NAND-based

 

Inputs		Outputs	
$\bar{r}$	$\bar{s}$	q_n	$\bar{q}_n$
0	0	?	?
0	1	0	1
1	0	1	0
1	1	q_{n-1}	$\neg q_{n-1}$



Other flip-flops


- **Derived from R-S**

- *Clocked R-S latch*

- Synchronous R-S latch variant
- Reacts to *r* or *s* signals while the clock signal is high

- *R-S master/slave (R-S flip-flop)*

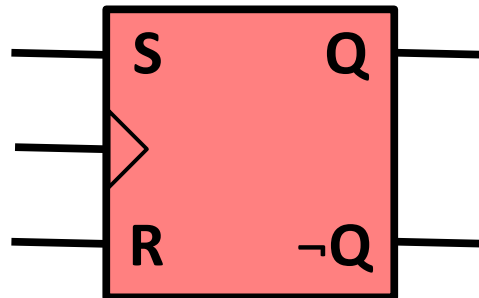- Reacts to *r* or *s* signals only on rising/falling edge of the clock signal



Other flip-flops (2)

- **Derived from R-S**

- *J-K master/slave (J-K flip-flop)*




- Extends R-S ($J = S$, $K = R$), inverts state when $J = K = 1$

- *Clocked D latch, D flip-flop*


- Value determines by single input

- *T flip-flop*


- Allows dividing clock signal frequency

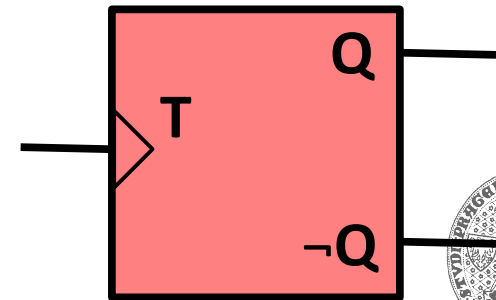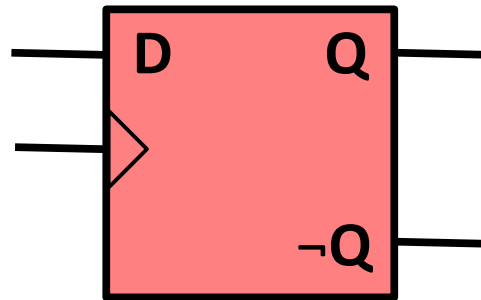 


Data register made of flip-flops

 

Shift register made of flip-flops

 

32-bit sequential multiplier

 

32-bit sequential divider

